



School of Computing  
Computer Science Program

CDA 3101

Introduction to Computer Logic

Assignment 7 - B

## Rubric

Student Name			
Assignment Name	Assignment 7 - Part B : Sequential State Machines Analysis and Design		
Assignment Checklist	Maximum Available Points	Received Points	Information
Waveform of State Machine using D-FF	30		Waveform via Multisim Grapher View. Must compare to state table.
Logic Diagram of State Machine using D-FF	30		Inputs and outputs clearly marked. Use clock with logic analyzer to prove proper operation. Use push-button for Reset
New State Table	20		Correctly populated state table
State Diagram	20		Diagram reflecting state table
Other Documents	NA		
Final Assignment Grade	Total =		

### **Notes for Scoring:**

**Note 1:** A final grade of “0” will be assigned if the circuit demonstration fails to work completely.

**Note 2:** Assignments will not be accepted late.

**Note 3:** Any assigned quizzes that are associated with this assignment will be taken on Bb unless otherwise noted.

**Note 4:** All submitted documents from MultiSim must contain the student’s name and UNF n-number printed via the software (insert text). No name and number; no points!!!!

**Note 5:** No "print screens" will be accepted from Multisim. Print all documents using the print function within the software.

**Assignment 7: Sequential State Machines**  
**Analysis and Design**  
**Part - B**

The purpose of this assignment is to give the student experience in analysis and design of a Mealy State Machines using D Flip-Flops.

**Equipment needed:**

Various TTL Gates and Flip-Flops  
Multisim Software

**Objectives:**

Perform the following using the state table and state diagram obtained from Assignment 7 Part A.

**A)** Redesign the state machine using the same D flip-flops. However, the input signals to the flip-flops will be from two 3x8 decoders (74138) and one 2x4 decoder (74139) plus any additional logic gates required. These three decoders will be connected in such a way as to operate like a 4x16 decoder. See Assignment 5 for a review if necessary.

The new state machine must also be designed as self-correcting for any unused state. For these states, the next state must point to state zero (0 0 0 0) with the Z output equaling zero. This condition must be reflected in your new state diagram and state table for this new design.

Use the TTL clock to feed the flip-flops, but be able to use a pushbutton as an alternative clock input if needed (see diagram). Also included a Reset / Clear switch.

This design will require a new, or modified, state table. Submit a copy of the state table, and state diagram for grading.

**B)** Build this new circuit using Multisim and confirm that operation of the circuit matches your state table and state diagram. . Printout the circuit and attach a copy for grading. Also submit a copy of the Multisim circuit.

**C)** Observe the waveforms of your new circuit to confirm that your designs are correct. Printout and submit the accompanying waveforms for this new circuit. Label all inputs and outputs on all waveforms through the Grapher. Ensure that all inputs and outputs are properly labeled on the logic diagrams as well.